

Design of a Miller compensated Two stage Op-amp with a single-ended output.


Input Stage	NMOS
Load	Capacitance = 2 pF


Name- Harshvardhan Singh

Roll no: 241040028

MVLSI IIT KANPUR



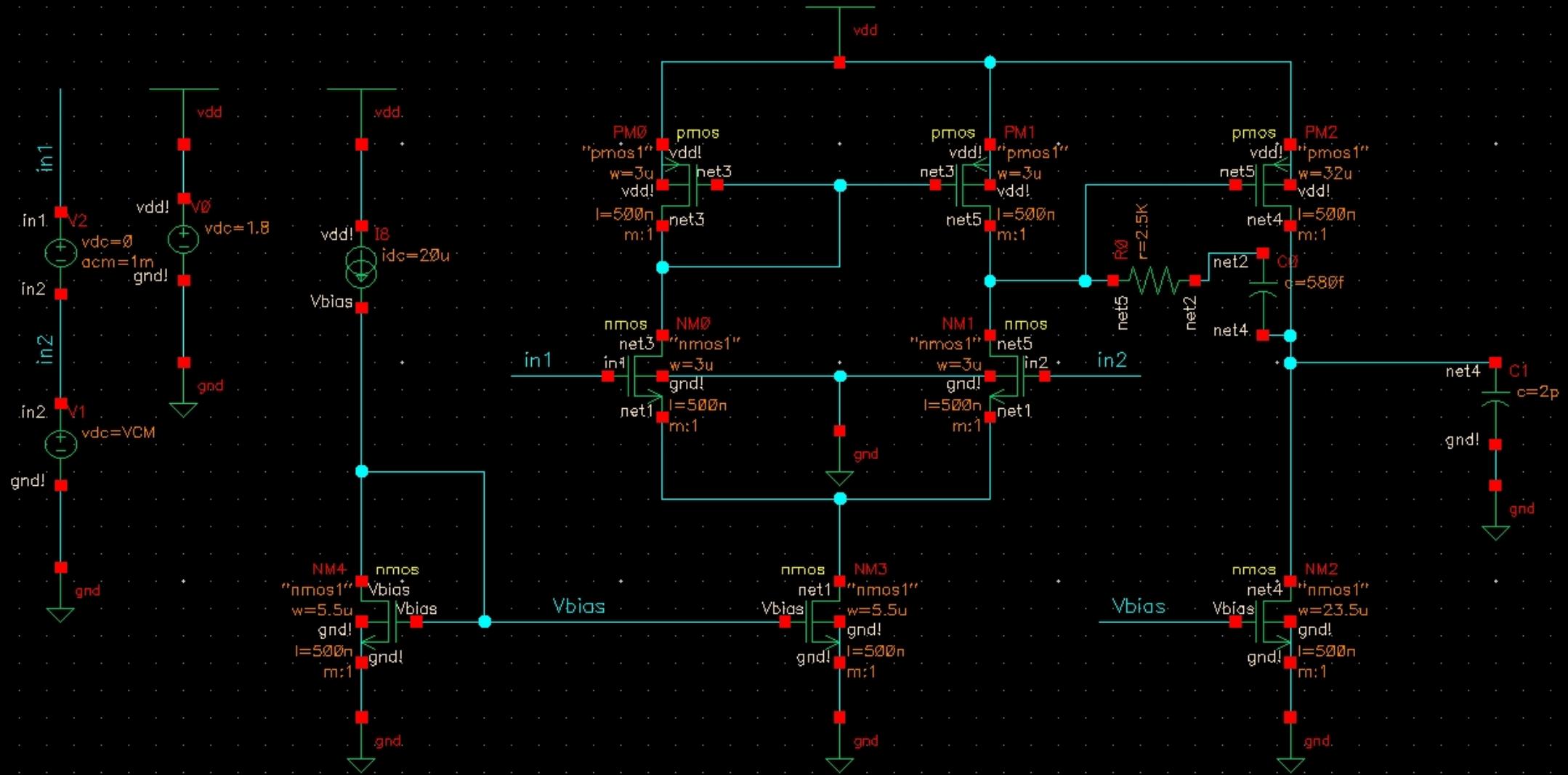

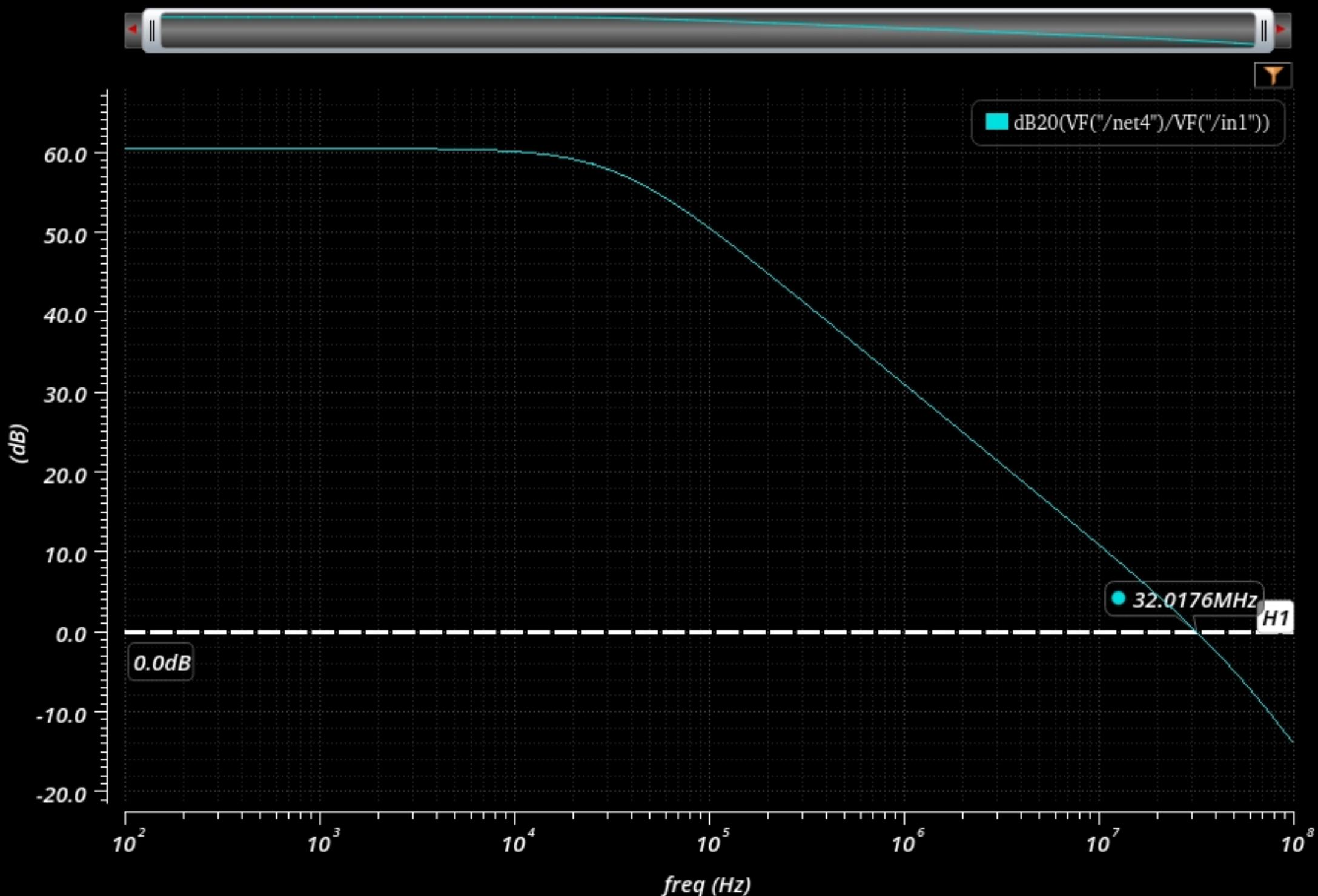


phaseDegUnwrapped((VF("/net4") / VF("/in1")))

1



V1

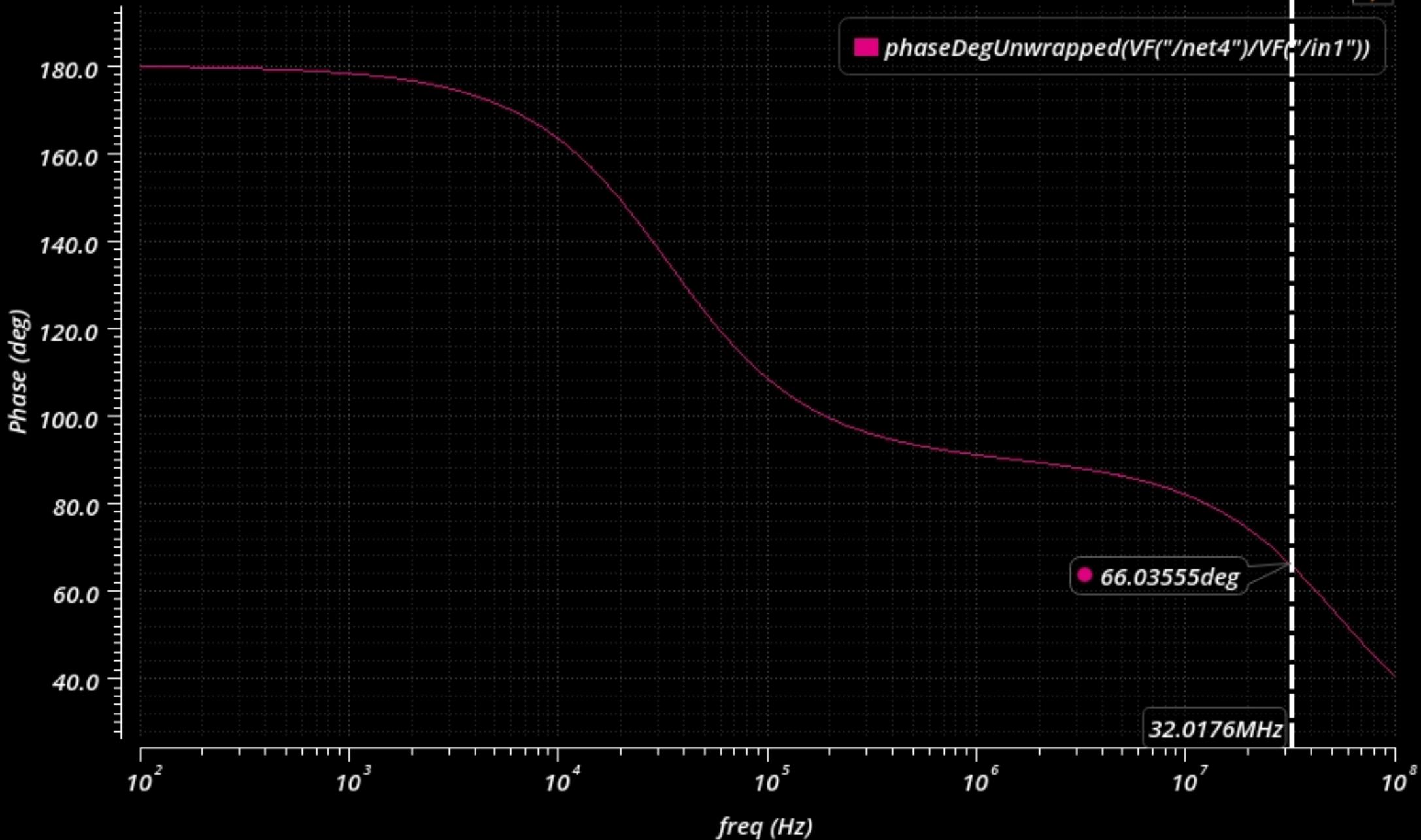


Outputs				
	Name/Signal/Expr	Value	Plot	Save
1	dB20(VF("/net4")/VF("/in1"))	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>
2	phaseDegUnwrapped(VF("/net4")/VF("/in1"))	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>
3	ymax(dB20((VF("/net4") / VF("/in1"))))	60.4605	<input checked="" type="checkbox"/>	<input type="checkbox"/>

\Rightarrow Specs.

- DC gain = 1000 $\Rightarrow 20 \log_{10}(1000) = 60 \text{ dB}$
- $G_{BW} = 30 \text{ MHz}$
- $P_M \geq 60^\circ$
- Slew rate = $20 \frac{\text{V}}{\mu\text{s}}$
- # $V_{DD} = 1.8 \text{ V}$
- Process = 180 nm
- $I_{CMR(+)} = 1.6 \text{ V}$
- $I_{CMR(-)} = 0.8 \text{ V}$
- $C_L = 2 \text{ pF}$
- Power $\leq 300 \text{ mW}$

We take $h \geq 2 \text{ hmin}$ here $\text{hmin} = 180 \text{ nm}$ (Tech)
 therefore $h = 500 \text{ nm}$.

Ckt.

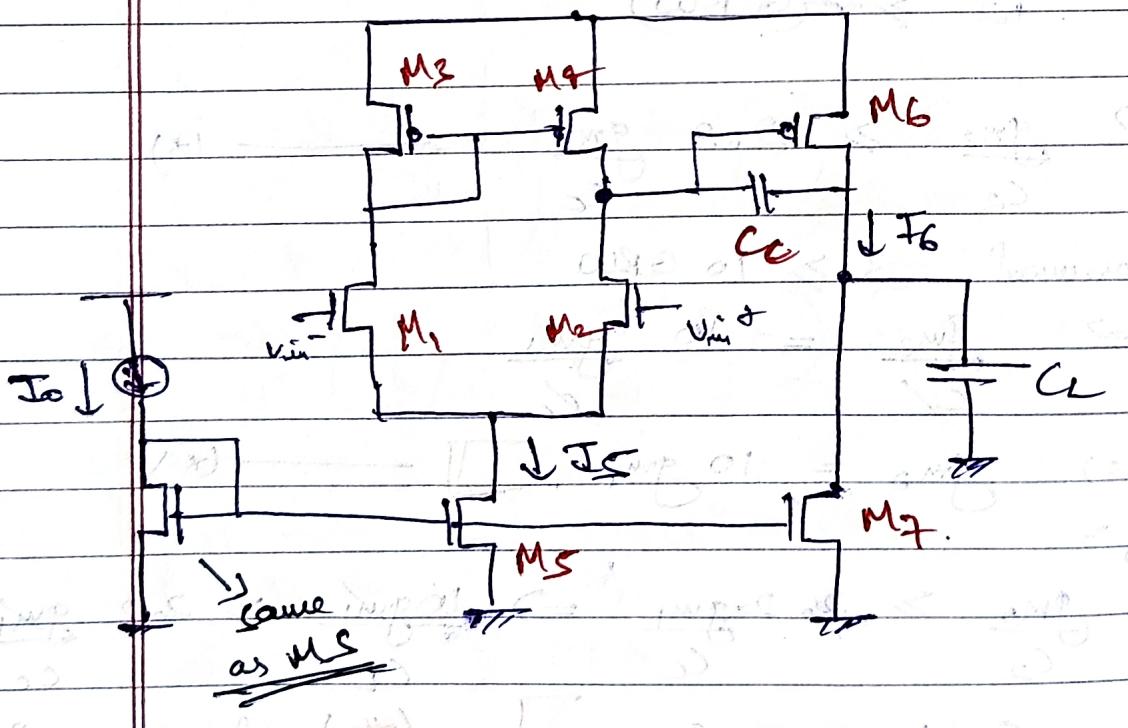

M_3 , M_4 from JCMR(+)

M_1, M_2 from GBW

$\cancel{M_5}$ I_S from slew rate.

M_5 from JCMR(-).

$$h = 500 \text{ nm} \quad \#$$

Since $PM \geq 60^\circ$ Then $C_C \geq 0.22 C_L$

$$\Rightarrow C_C \geq 0.44 \text{ pF}$$

$$\Rightarrow C_C \geq 440 \text{ fF}$$

Thus using $C_C = 800 \text{ fF}$. $\#$

Since $SR = 20 \frac{\text{V}}{\mu\text{s}} = \underline{I_S} \Rightarrow \underline{I_S}$

$$\Rightarrow I_S = \left(\frac{20 \text{ V}}{\mu\text{s}} \right) (800 \text{ fF})$$

$$\Rightarrow I_S = 16 \mu\text{A}$$

Thus $\Rightarrow I_S = 20 \mu\text{A}$. $\#$

\Rightarrow Design of M_1, M_2 .

$$g_{m1} = (g_B)(2\alpha) C_C$$

$$= (30 \text{ MHz})(2\alpha)(800 \text{ fF})$$

$$\Rightarrow g_{m1} = 150.79 \text{ m}\left(\frac{\text{A}}{\text{V}}\right)$$

Thus, $g_{m1} = 160 \frac{\text{mA}}{\text{V}}$. $\#$

$$\text{Now, } \left(\frac{w}{L}\right) = \frac{gm^2(1)}{(M_{\text{on}})(2J_D)}$$


$$\text{Here } J_D = \frac{J_S}{2} \Rightarrow 10 \mu\text{A}$$

$$\Rightarrow \left(\frac{w}{L}\right) = \frac{(160 \mu)^2}{(300 \mu)(20 \mu)} = 4.44$$

Thus $\boxed{\left(\frac{w}{L}\right)_{1,2} = 4.44}$

→ Design M₃, M₄.

drawing only half ch.

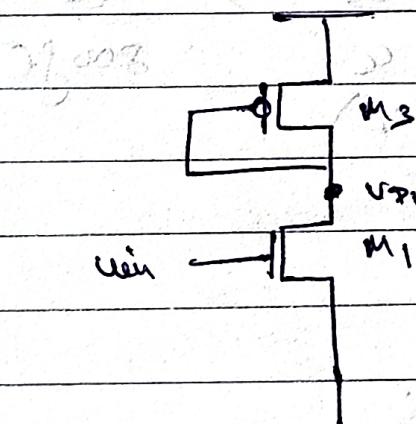

then if $V_{in} \uparrow$ then M₁
will enter triode they,
 $V_{in} > V_{gs1} - V_{th1}$

$$\Rightarrow V_{gs1} \leq V_{D1} + V_{th1}$$

$$\Rightarrow V_{in} \leq V_{D1} + V_{th1}$$

$$\Rightarrow V_{in} = V_{D1} + V_{th1}, \quad \rightarrow (*)$$

$$\& V_{D1} = V_{DD} - V_{sg2} \quad \rightarrow (**)$$

then,

$$J_B = \frac{M_{\text{on}}}{2} \left(\frac{w}{L}\right) \cdot (V_{gs} - V_{th})^2$$

$$\Rightarrow \left(\frac{M_{\text{on}}}{2}\right) (V_{gs} - V_{th})^2$$

$$\Rightarrow V_{GS} = \sqrt{\frac{2I_2}{B_p}} + |V_{DH3}| \quad \text{--- (a)}$$

thus,

$$V_D = V_{DD} - \left[\sqrt{\frac{2I_2}{B_p}} + |V_{DH3}| \right]$$

Since

$$\underbrace{V_{in}}_{\text{max}} \leq V_D + V_{DH1}$$

JCMR(+)

$$\Rightarrow JCMR(+) \leq V_D + V_{DH \min}$$

thus,

$$JCMR(+) \leq V_{DD} - \sqrt{\frac{2I_2}{B_2}} - |V_{DH3}|_{\min} + V_{DH \min}$$

$$\text{thus, } \Rightarrow \frac{2I_2}{B_2} = \left(V_{DD} - JCMR(+) - |V_{DH3}|_{\min} + V_{DH \min} \right)^2$$

~~$\mu_{pcon} = 60 \mu A/V^2$~~

$$\Rightarrow \frac{2I_2}{(\mu_{pcon}) \left(\frac{w}{L} \right)} = \left(V_{DD} - JCMR(+) - |V_{DH3}|_{\min} + V_{DH \min} \right) \quad \text{from sim, diff amp}$$

$$\Rightarrow \left(\frac{w}{L} \right) = \left(\frac{2I_2}{\mu_{pcon}} \right) \left(\frac{V_{DD} - JCMR(+) - |V_{DH3}|_{\min} + V_{DH \min}}{10^6} \right)^2$$

thus to find out the values of V_{DH} we will have an exact replica of the diff-amp. ckt.

Schematic \Rightarrow 3-1-freq - 2stage-gpamp.

Photo \Rightarrow 3-1-freq - 2stage-gpamp.

at $V_{CM} = 0.6V$.

$$V_{DH1} = \frac{549mV}{6.37mV}$$

$$|V_{DH}| = +458mV$$

at $V_{CM} = 0.8V$

$$V_{DH1} = 549mV$$

$$|V_{DH}| = +458mV$$


$$\mu_{pcon} = 470 \mu A/V^2$$

$$549mV$$

using these we get

$$\left(\frac{w}{l}\right) = \frac{4.023}{3.4} \approx \underline{\underline{6}}.$$

\rightarrow Design of M_S.

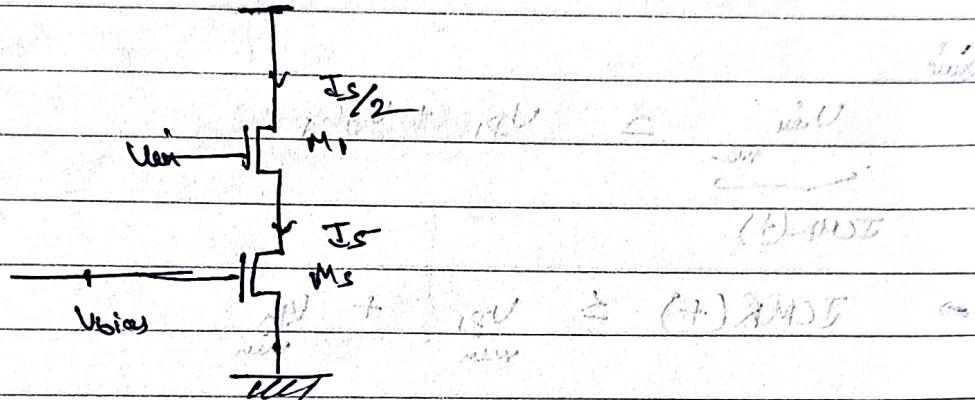

If $V_{in} \downarrow$ then $V_{gs1} \downarrow$ thus, $V_{DS} \downarrow$.

$$V_{DS} > V_{GS} - V_{THS}$$

Thus as $V_{DS} \uparrow$ then M_S ages in time.

Thus, $V_{in} \geq V_{GS} + V_{DSAT}$ (V_{DSAT} above which min. current).

$$JCMR(-) \geq V_{GS} + V_{DSAT}$$

$$\Rightarrow JCMR(-) \geq \left(\frac{2ID}{\delta_1} + V_{th1} \right) + V_{DSAT}$$

$$V_{DSAT} \geq JCMR(-) - \sqrt{\frac{2ID}{\delta_1}} - V_{th1}$$

$$\Rightarrow V_{DSAT} \geq 0.09 - \sqrt{\frac{2 \times 10^{-4}}{360 \mu A}} - 0.7$$

$$\Rightarrow V_{DSAT} \geq 0 - \text{unseen} \text{ thus increases (to)}$$

$$\text{making } \left(\frac{\omega}{L}\right)_{1,2} = 6 \quad \boxed{\#}$$

$$\text{we get, } v_{TSEAS} = 10.4 \text{ m/s.}$$

Thus, $\left(\frac{\omega}{L}\right)_S = \frac{2\pi D^{200}}{(gm_s)(v_{TSEAS})^2} \Rightarrow \frac{3600}{10.4^2} \boxed{10.22}$

$$\Rightarrow \boxed{\left(\frac{\omega}{L}\right)_S = 10.27. \quad \boxed{\#}}$$

Design of M6.

For $PM \geq 60^\circ$ we make one assumption.

$$Z \geq 10 \text{ GBW}$$


$$\Rightarrow gm_S \geq 10 \text{ gm}_1 \rightarrow \underbrace{152.4 \mu}_{\text{from sim.}}$$

Thus,

$$\Rightarrow gm_S \geq 10 \times 160 \mu \rightarrow \underbrace{1600 \mu}_{\text{assume}} \quad \boxed{*}$$

$$\Rightarrow gm_S \geq 1600 \mu. \quad \boxed{*}$$

Then,

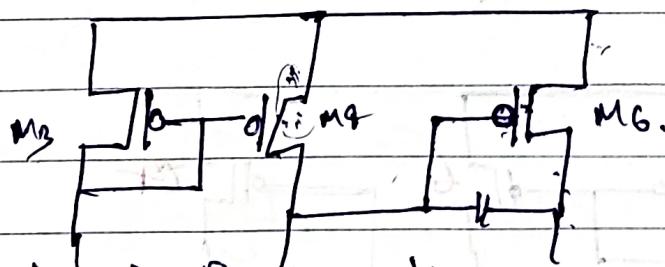

If proper working then $V_{GE3} = V_{GCF} = V_{GFS}$.

Thus $\left(\frac{\omega}{L}\right)_B = \frac{I_E}{I_T} = \frac{gm_S}{gm_B}$ we have $gm_B = 150 \mu$
 from sim.

$$\Rightarrow \boxed{\left(\frac{\omega}{L}\right)_S = \left(\frac{1600}{gm_B}\right) \left(\frac{\omega}{L}\right)_T \Rightarrow 64 \quad \boxed{\#}}$$

Ans,

$$\frac{J_6}{J_4} = \frac{(w/L)_6}{(w/L)_4}$$

$$\Rightarrow J_6 = \left(\frac{64}{6} \right) (10)$$

$$\Rightarrow J_6 = 106.66 \text{ mA.}$$

Design of M7.

Ans Is flow through M7.

Ans,

$$\frac{(w/L)_7}{(w/L)_5} = \frac{J_7}{J_5}$$

$$\Rightarrow \left(\frac{w}{L} \right)_7 = \left(\frac{106 \text{ m}}{204} \right) (11)$$

$$\Rightarrow \left(\frac{w}{L} \right)_7 = 58.3$$

$$\Rightarrow \boxed{\left(\frac{w}{L} \right)_7 = 59} \quad \text{#}$$

